


Term Project MPI

Group 2: Microwave Oven

R. Ramanathan
Vishal Sharma
Sarthak Chaudhary
Abhishek Jaswal
Arunaabh Singh
Akshat Mahajan


2019A7PS0115G
2019A7PS0036G
2019A7PS0125G
2019A8PS0647G
2019A8PS0664G
2019A8PS0687G

8284: Timing Signal Generator

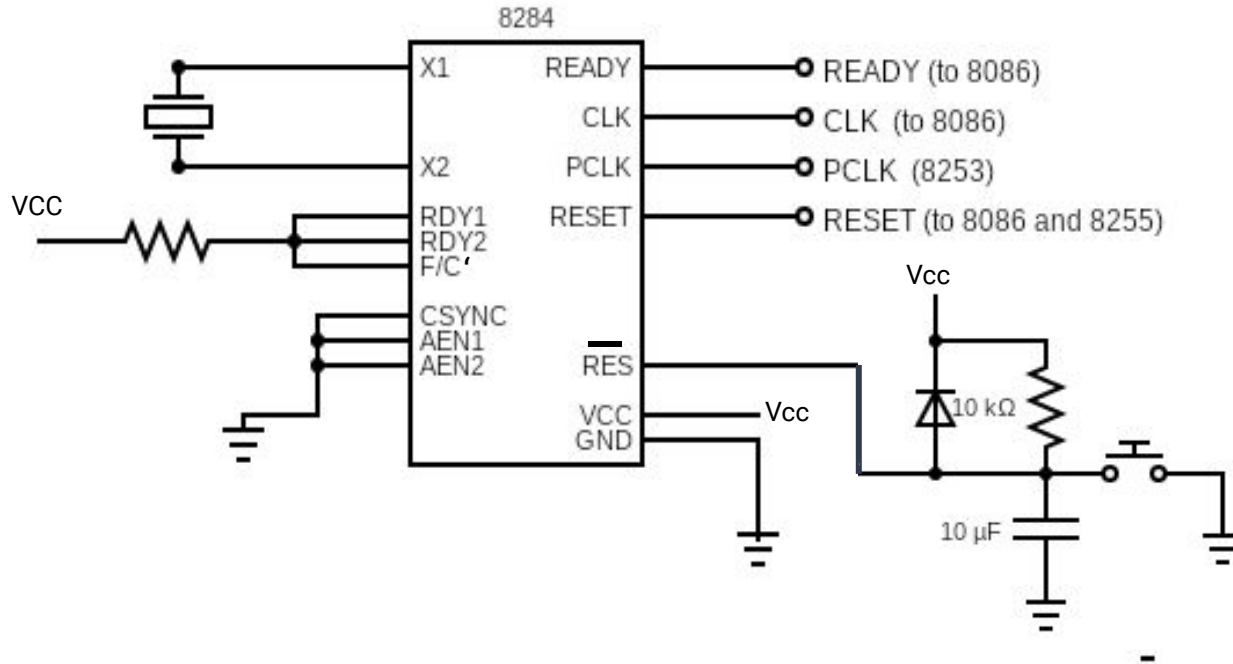

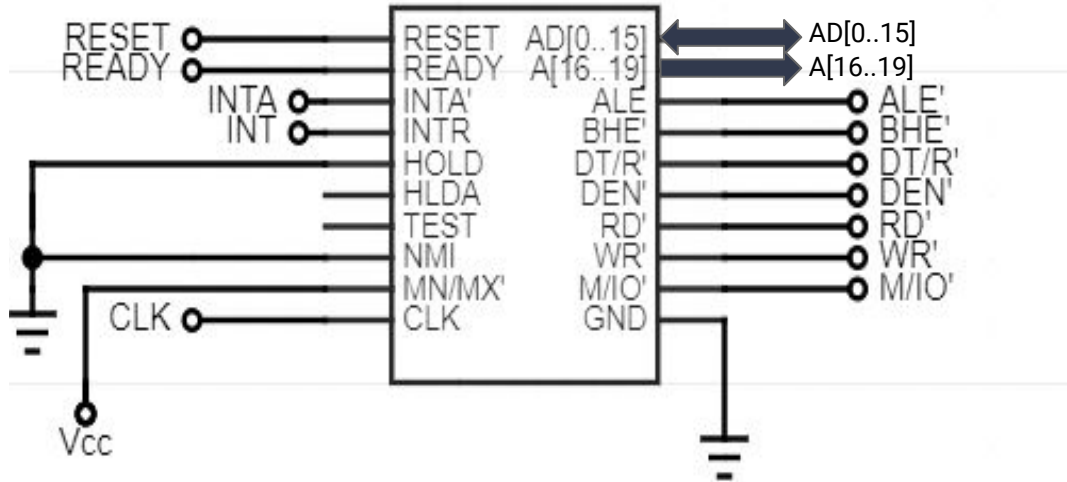
- The Crystal used is of 15 MHz.
- The pins ASYNC, EFI and OSC have not been depicted as they are not required for our design.



8086 pin out




 
- Reset and Ready are given by the 8284
- The CLK signal also comes from the 8284 at 5 MHz
- We are not using NMIs and the INTR and INTA' are connected to the 8259
- VCC and VDD are not depicted here, but are both connected to +5V.
- HLDA and TEST don't have any connections



ADDRESS LINE DEMULTIPLEXING




- The ALE signal comes from the 8086
-  Coming in from the 8086
-  Going out from the octal latch to be used in MEM and I/O access.

  DATA LINE DEMULTIPLEXING




- The DEN' and DT/R' signals comes from the 8086
-  Coming in from the 8086
-  Going out from the octal latch to be used in MEM and I/O operations.



Memory Decoder

 

I/O Decoder

 


Control Signals

 
 


The LS244 buffer does not alter the signal and is always active



Bank Signals

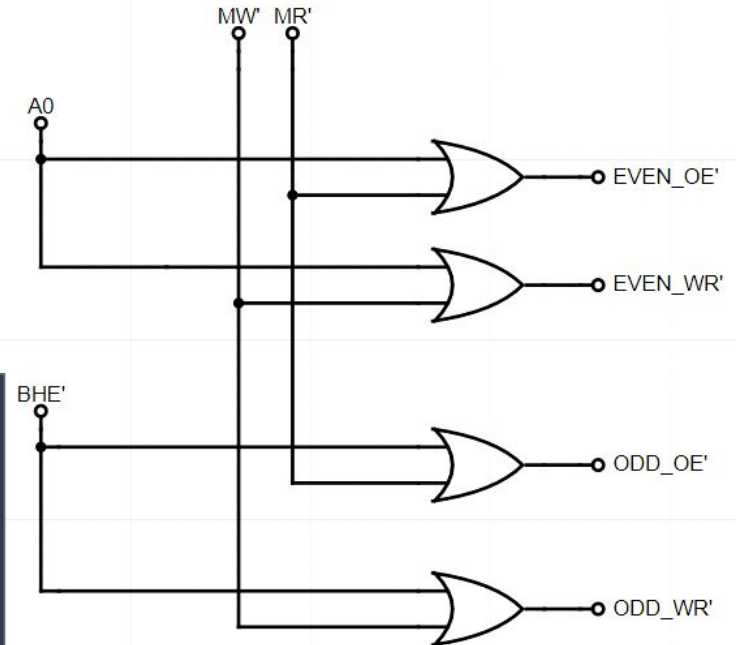



ROM 1

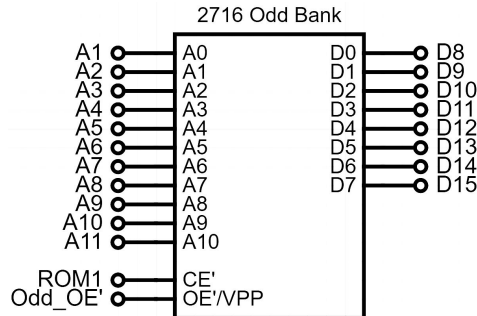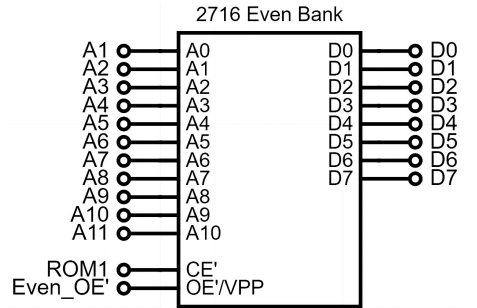


ROM 2

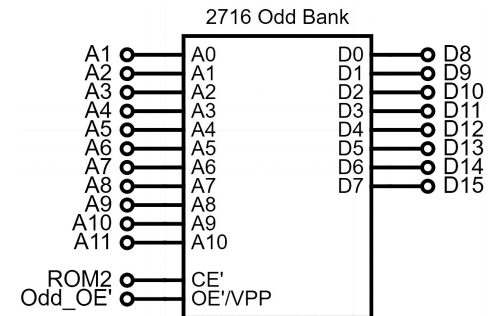 

RAM

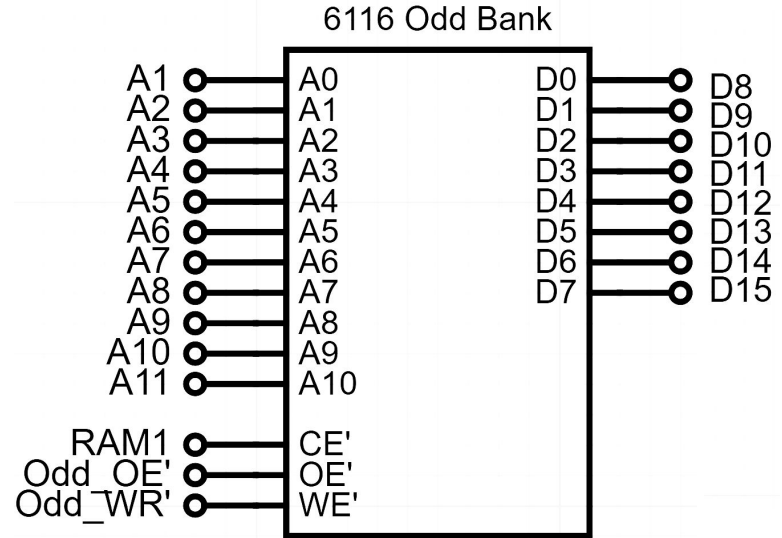 


8259 interfacing

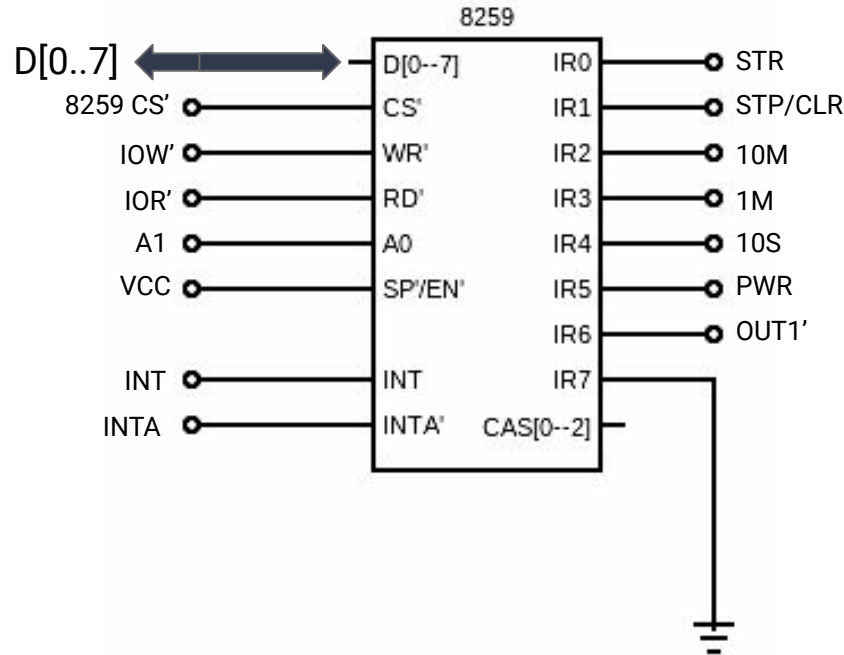


- The CS' is coming from the I/O decoder circuitry
- INT and INTA' are directly connected to the 8086
- CAS[0..2] is not used as there is only 1 8259 in the system
- IR0-5 are connected to their respective buttons
- IR6 is the OUT1' from the 8253 acts as the 1HZ signal for the timer ISR
- IR7 is not used, hence Grounded and masked

8253 interfacing

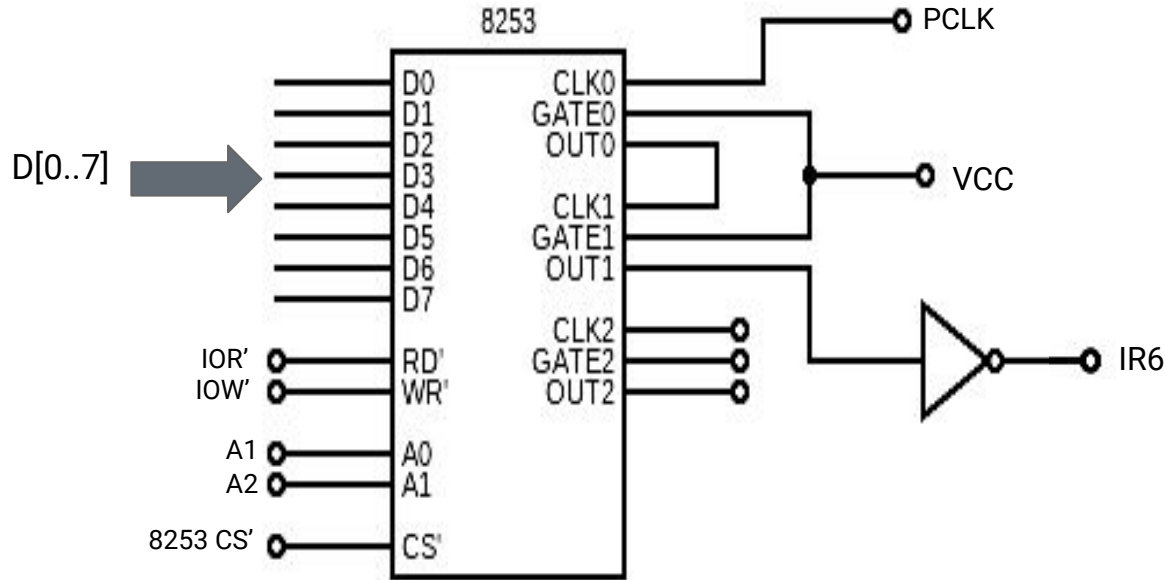


- The CS' is coming from the I/O decoder circuitry
- The $PCLK$ is the 2.5 MHz signal from the 8284
- The $IR6$ is going to the 8259
- $CLK2$ and its respective gate and output are not in use

8255

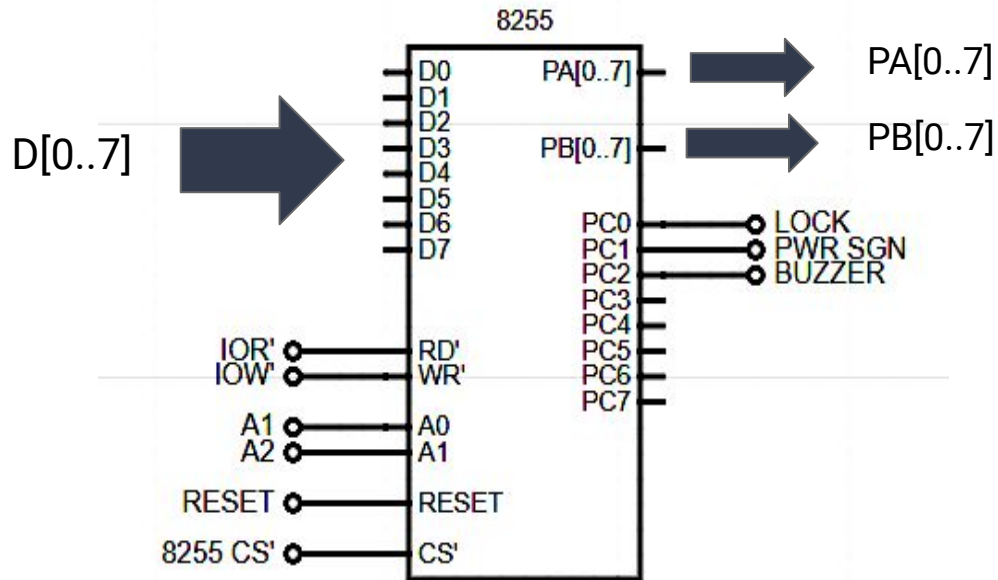


- The CS' is coming from the I/O decoder circuitry
- RESET is coming from 8284
- Port A and Port B are connected to the 7 Seg displays
- Port C is being used in BSR mode
- PC0 is controlling the lock
- PC1 is providing the signal at the requested Power Level
- PC2 is controlling the buzzer when required.

7 SEG

 



- This is the MSB of the timer/power level display
- The other 7 Seg displays are connected similarly with PA[4..7], PB[0..3] and PB[4..7]
- The Ports A and B are always active and controlled in the MAIN loop
- The decimal point(dp) pin is not connected to anything

Command Buttons & Door Check Button

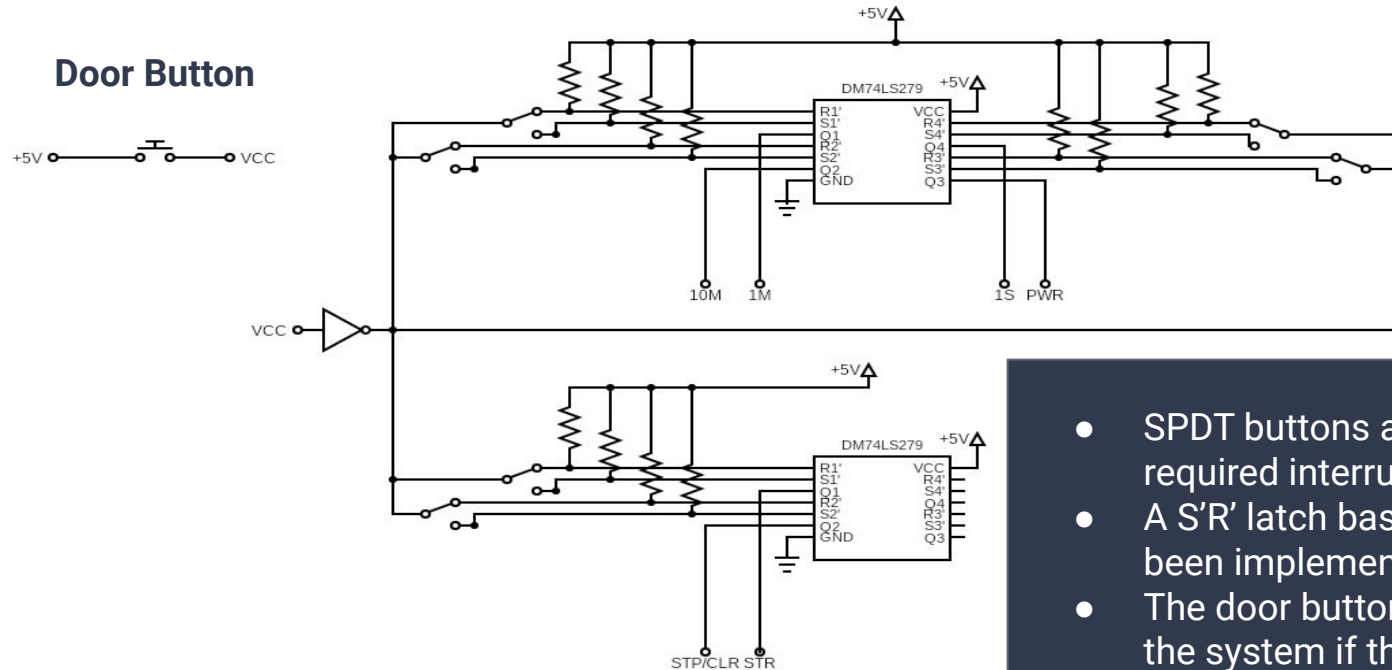

- SPDT buttons are being used to raise the required interrupts to the 8259
- A S'R' latch based debounce circuitry has been implemented for the buttons.
- The door button connects the powerline to the system if the door is closed and contact is made.

Buzzer & Lock

  

- The SN74AUC1G126 Tri State buffer is used to provide the required voltage to the output devices
- The Buzzer power is controlled by the PC2 port of 8255
- The Lock power is controlled by the PC0 port of 8255